
 


 Sol.1 (a) MOD-60 counter is used to divide time by 60.




Sol.1 (b)




Sol.1 (c) P – D_{in} Q – s₂ R – s₀ S – s₁

Sol.1 (d) CMOS as EX-OR gate:

 


Sol.2(a)

Q ₂	Q ₁	Q ₀	J ₂	k ₂	J ₁	k ₁	J ₀	k ₀
0	0	0	0	x	0	x	1	x
0	0	1	0	x	1	x	x	1
0	1	0	1	x	x	1	0	x
1	0	0	x	0	0	x	1	x
1	0	1	x	0	1	x	x	1
1	1	0	x	1	x	1	0	x

 

$J_2 = Q_1$

 

$k_2 = \bar{Q}_2$

$Q_1 Q_0$	00	01	11	10
Q_2				
0		1	X	X
1		1	X	X

$$J_1 = Q_0$$

$Q_1 Q_0$	00	01	11	10
Q_2				
0	1	X	X	•
1	1	X	X	•

$$J_0 = \bar{Q}_1$$

$Q_1 Q_0$	00	01	11	10
Q_2				
0	X	X	X	1
1	X	X	X	1

$$k_1 = 1$$


$Q_1 Q_0$	00	01	11	10
Q_2				
0	X	1	X	X
1	X	X	X	X

$$k_0 = 1$$

Sol. 2(b)

This is standard R-S FF or Latch

R	S	Q_{n+1}	\bar{R}	\bar{S}	Q_{n+1}
0	0	Q_n	1	1	Q_n
0	1	1	1	0	1
1	0	0	0	1	0
1	1	??	0	0	??

 

Sol.3(a)





E	Data - In	X (address)	Q_{n+1}	Data Out
0	X	X	0	0
1	0	X	0	0
1	1	1	1	1
1	1	0	0	0

Sol.3(c)


YZ	00	01	11	10
X				
0	0			0
1	0		0	

$$F = (X+Z)(X+Y+Z)(Y+Z)$$

Sol.4 (a)

    

 Sol.4 (b) Full subtractor is designed by use of 9 gates.



Sol.4(c)

Q_2	Q_1	Q_0	Y_7	Y_6	Y_5	Y_4	Y_3	Y_2	Y_1	Y_0	\bar{P}_r	$\bar{C}l_r$	\bar{Q} (up)	Q(Down)
0	0	0	1	1	1	1	1	1	1	0	1	0	1	0
0	0	1	1	1	1	1	1	1	0	1	1	1	1	0
0	1	0	1	1	1	1	1	0	1	1	1	1	1	0
:				:					:			:		:
1	0	1	1	1	0	1	1	1	1	1	0	1	0	1

Down counter starts row. Sequence: 0, 1, 2, 3, 4, 5, 4, 3, 2, 1, 0, 1, 2, 3.

Sol.5 (a) Quantization error = $\frac{1}{2^N - 1}$ where $N = 12$

$$\text{Error} = \frac{1}{2^{12} - 1} = 0.025\%$$

Sol.5 (b) $2V \rightarrow +127$ $-2V \rightarrow -128$


$$-1.5 \rightarrow \frac{-128}{2} \times 1.5 = -96$$

$$\begin{array}{r} 96 \rightarrow 01100000 \\ \downarrow \\ 10011111 \\ + \quad 1 \\ \hline 10100000 \\ \downarrow \\ \text{A0H} \end{array}$$

Sol.5 (c) Range will be: (2000 – 3FFF)

A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	A_{10}	-----	A_0
0	0	1	0	0	0	-----	0
0	0	1	1	1	1	-----	1




Sol.5 (d)

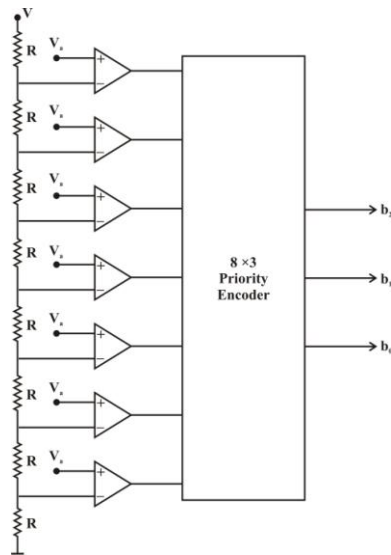

Sol.6 (a)

Logic Family	Propg.delay(ns)	Power dissipation (mW)	Fan-in	Fan-out	Noise margin
RTL	12-30	15	4	4	0.2-0.4
DTL	30	12	10	8	0.7
TTL	5-15	10	8	10	0.4
ECL	2-4	50	5	16-20	0.4
I ² L	1	0.1	5	8	0.35
PMOS	50	1	8	20	0.4
CMOS	70	0.01	8	50	5

Sol.6 (b)

  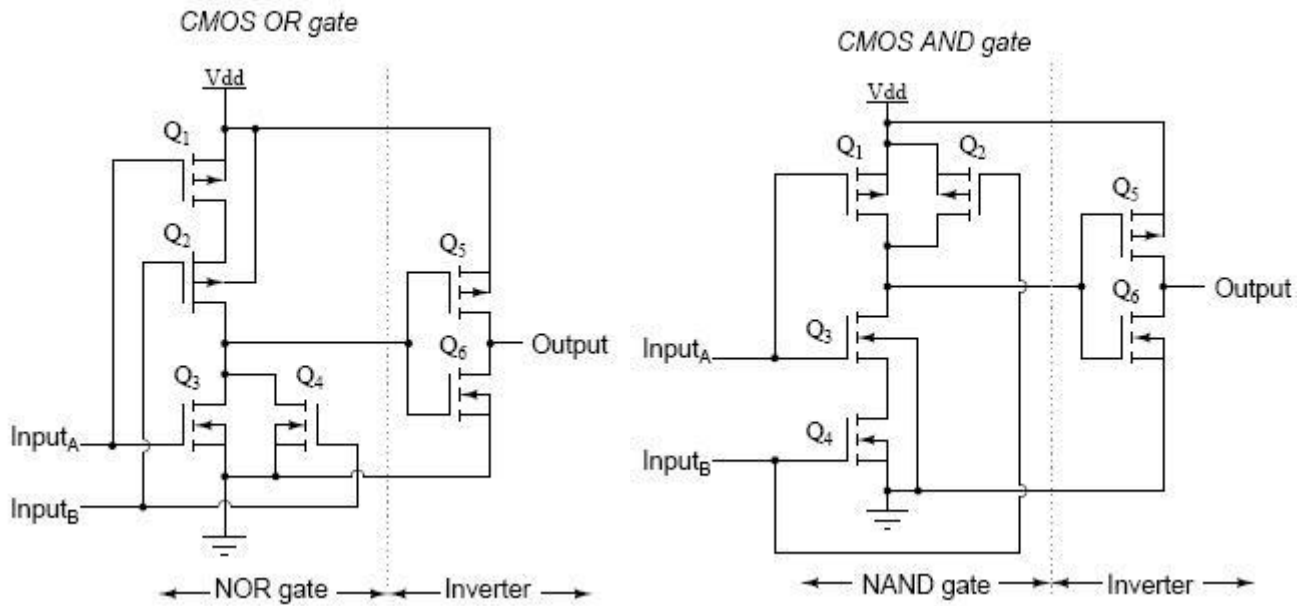

Sol.6 (c)

Case-1: when control input is Low:

When one of the input of emitter of Q₁ is LOW whatever may be data input Q₃ and Q₂ to turn off. Here both Q₃ and Q₄ in totem pole are off and output of circuit behaves like an open circuit with a very high output impedance.

Case-2: when control input is High:

- (i) when data input is Low: Output is high
- (ii) when data input is High: Output is low

Sol.7 (a) Q_n = 1 B = 0

Initially Q_n=0=A=B

After 1 clock cycle output of FF will be 1 and counter will be enable and A=0 and B=1

After 2 clock cycle output of FF will be 0 and counter will be disable and A=0 and B=1

After 3 clock cycle output of FF will be 0 and counter will be disable and A=1 and B=0

Sol.7 (b) Here $Y=X+1$ and if base is r then $rX+Y=25$ and $rY+X=31$

By solving all 3 equations

$$\text{Base}(r) = 7 \quad X = 3 \quad Y = 4$$

Sol.7 (c) $(5000-57FF)H$

Sol. 7(d)

